## Blue LED for Drake 7-Line and the C-Line

The standard lamps in the old Drake-rigs are not the optimum for the blue foils in the meterand frequency-scales. Some OM's propose to replace them by blue LED's.

7-Line: TR-7, R-7 and RV7:

In the TR-7 (also R-7 and RV-7), it can rather easily be done, because the lamps are fed with 12VDC. The circuit is shown in picture 1. 3 LED's and one resistor (330-Ohm) are in series.



Picture 1: Schematic for TR-7, R-7 and RV7

Totally 6 LED's are used for an optimum illumination of the scale and meter.



Picture 2: TR-7 and R-7, Meter-illumination

## Modification of the LED's:

The original LED's had a rather good focussing lens which resulted in bright and small spots in the illuminated scale. Therefore i recommend to remove the lens with a file or rasp and to make the surface rough to have a good diffusing effect (picture 3).



Picture 3: Modification of the LED's

Picture 4 and 5 show the modified LED's in place (TR-7 and R-7).



Picture 4 and 5: TR-7 and R-7, LED's for meter-illumination

The whole circuit is soldered onto a small piece of an experimental board. The clamps of the original sockets of the bulbs are used now as fixture for the LED's. The 12VDC-supply is taken from the same pins, the original lamps had been connected to.

The LED's should be arranged and bended for an optimum and evenly illumination.

The illumination of the frequency-scale of the PTO's requires a little bit more care, because the small board could interfere with the PTO-gear (lever) – see picture 6!



Picture 6 and 7: Illumination of the PTO in the RV7 (similar in the TR-7 and R-7) The board is fixed with some drops of glue.

## C-Line: R-4C and T-4XC:

The easiest way is to simply exchange the lamp by LED's with an additional series resistor – but this would cause the LED to flicker with 50Hz/60Hz (halfwave). A LED should be connected to DC, so i propose to use a circuit like this (picture 8):

Bridge rectifier NonF 172V 22052 2x LED 6,3 VAC 0- -4x 4007 22052 0 ULTIMO 12/07

Picture 8: Schematic

The 6.3VAC is rectified (fullwave) and smoothed by an electrolytic capacitor. The resulting DC-voltage is sufficient for two LED's in series with 220 Ohms.

The whole circuit is soldered onto a small piece of an experimental board. The clamps of the original sockets of the bulbs are used now as fixture for the LED's. The board can be soldered to this clamp. The original wires for the bulbs (6.3VAC) can now be used for this circuit.



Picture 9: Meter illumination

For the meter, only two LED's are sufficient (picture 9).



Picture 10: Frequencyscale illumination



Picture 11: Diffusor LED's

For a better and more constant illumination of the whole frequency-scale, i used 4 LED's with two series resistors (2 LEDs with one resistor acc. Picture 1). The LED's should be arranged and bended for an optimum and evenly illumination - see pictures 10 and 11.

In my second R-4C, i used a different construction (pictures 12, 13 and 14). The 4 LED's are arranged parallel and the hole in the reflector of the frequencyscale had to be made bigger.

Pictures 11, 12 13: Alternative construction

## These are the results:





If you want to contact the author: Stefan Steger, DL7MAJ, eMail: <u>dl7maj@darc.de</u> Homepage: <u>www.dl7maj.de</u>

.-.-. ... -.-