


## Panoramaadapter for the Drake R7

### Introduction

Wanted to connect a panorama adapter to my R7 and looked through the schematic where the best point for the tap could be and which other signals are needed for that.
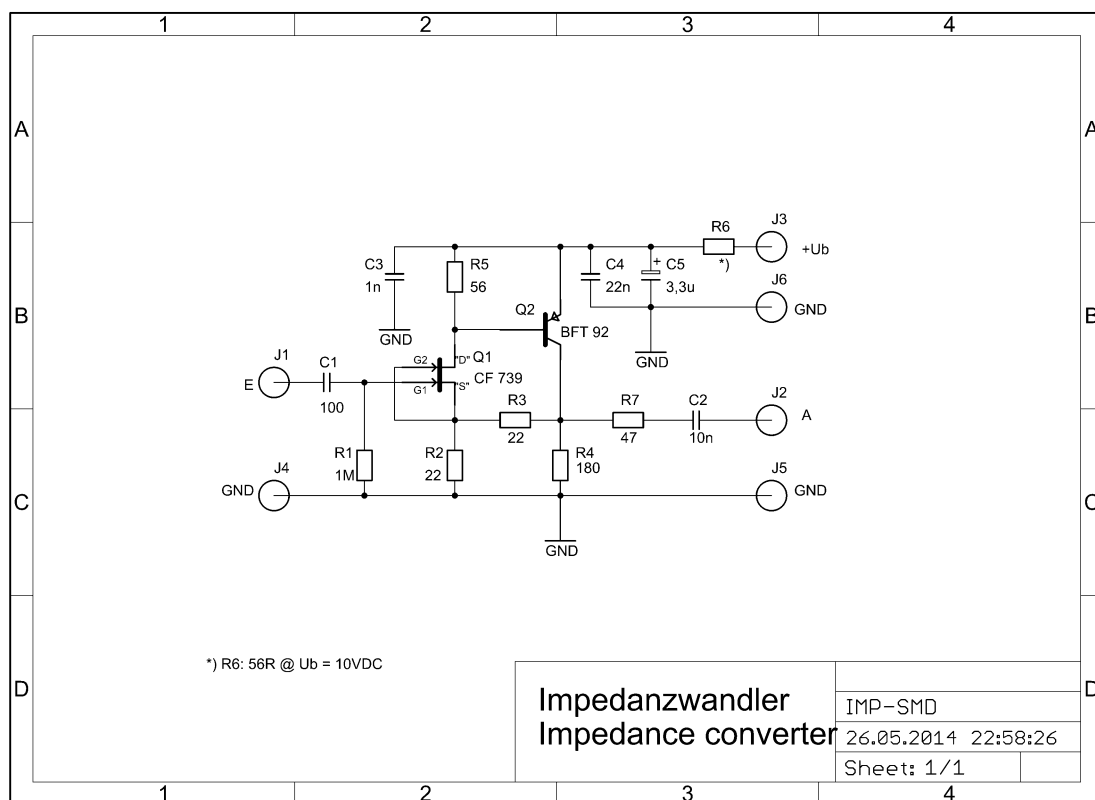
### SMD-Impedance Converter

The first thing to do was to design a small impedance converter to tap the HF signals. The voltage gain should be 1, the input impedance 1M $\Omega$  and the output impedance 50  $\Omega$  for direct connection of coaxial cables. Pictures 1 and 2 show the result. This circuit is built with SMD.




Picture 1 Schematic of Buffer Amplifier (SMD)

### Tap for the 1<sup>st</sup> IF (48,05MHz)

The 7-Line has a rather narrow roofing filter (app. 15kHz), therefore the tap of the IF has to be in front of this filter to achieve a possible span width of several 100kHz for complete ham bands. The only possible point to tap is the 1<sup>st</sup> IF (48,05MHz) on the Up-Converter board at Q402/T402 (picture 3). To avoid any parasitic oscillations a ferrite bead (FB) and a 100 $\Omega$  resistor is proposed. Picture 4 shows the installation.

Pin 4/16 is not used in the R7 and therefore available for this purpose. On the motherboard at pin 4/16 a coaxial cable is connected and fed to the rear of the R7 (picture 5 and 9).

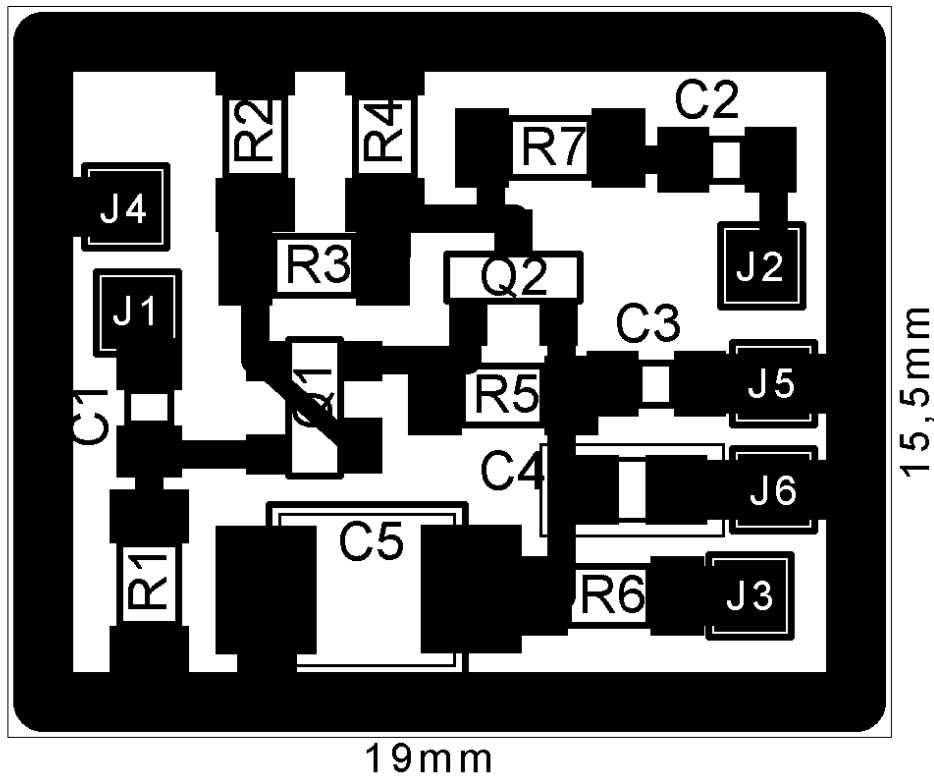Note: In the TR7 this pin 4/16 and all others are used for the TX-path and this requires an additional output on the Up-Converter board in the TR7.



Picture 2 Layout of Buffer Amplifier (SMD)



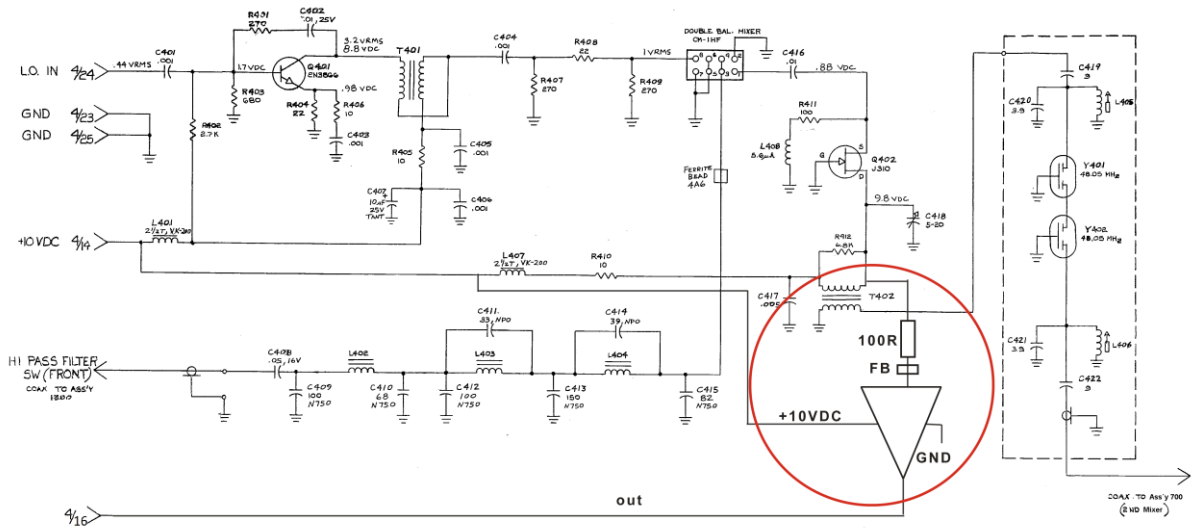


Fig. 2-8 Up-Converter Board Schematic

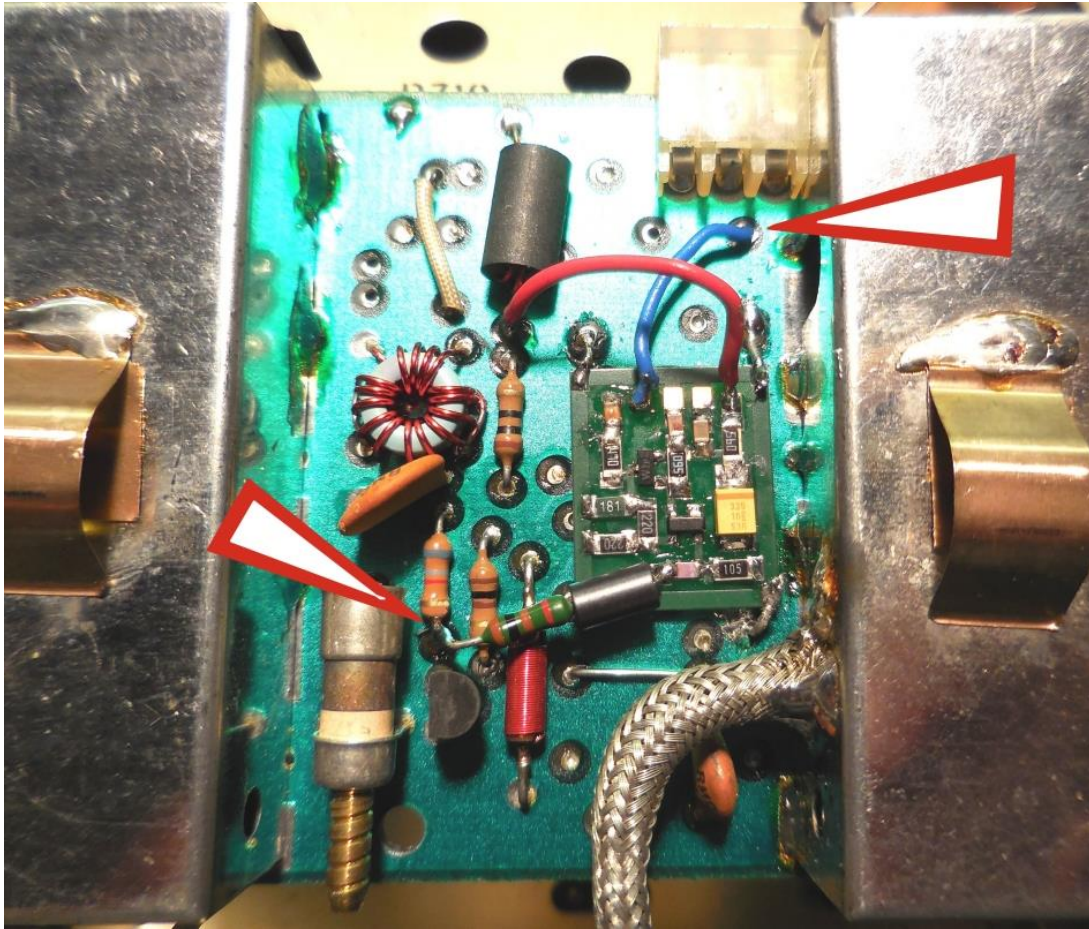Picture 3 Connection of output 1<sup>st</sup> IF



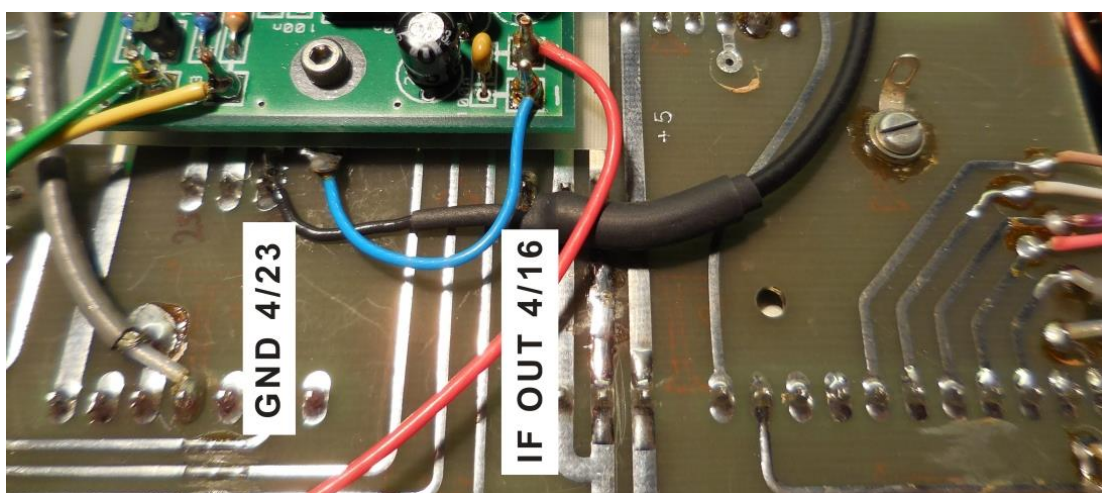
Picture 4 Installation of Buffer for 1<sup>st</sup> IF



Picture 5 Output of 1st IF (the other board is the DAFC)

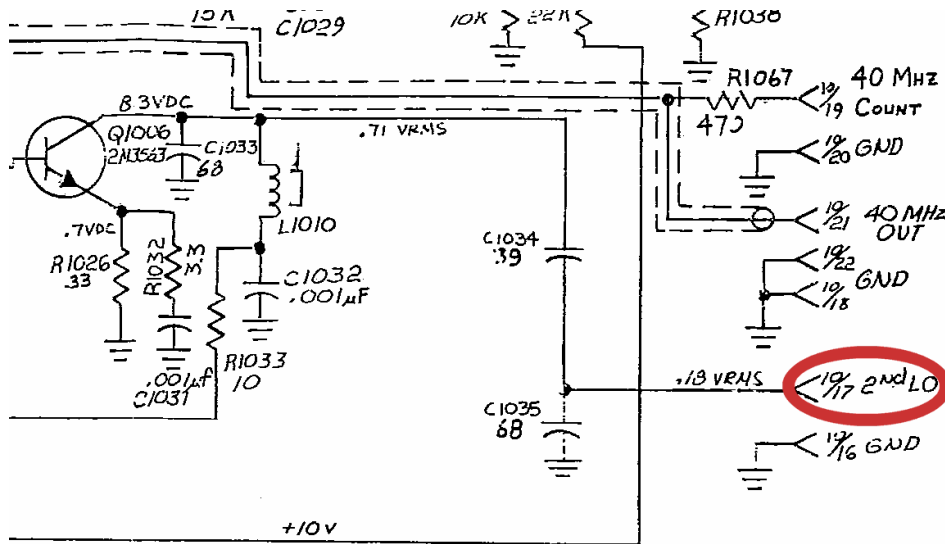
### Tap for the 2nd LO (53,695MHz)

The 1<sup>st</sup> IF (48,05MHz) is sometimes too high for available panorama adapters; this requires a down conversion. The easiest way is to use the internal 2<sup>nd</sup> LO (53,695MHz), which converts the 1<sup>st</sup> IF down to 5,645MHz in the 2<sup>nd</sup> mixer. The 2<sup>nd</sup> LO can be tapped at pin 10/17 on the PBT/Reference Board (picture 6 and 7).




Part of  
Fig. 2-20 PBT/Reference Board Schematic

Picture 6 Output of 2<sup>nd</sup> LO

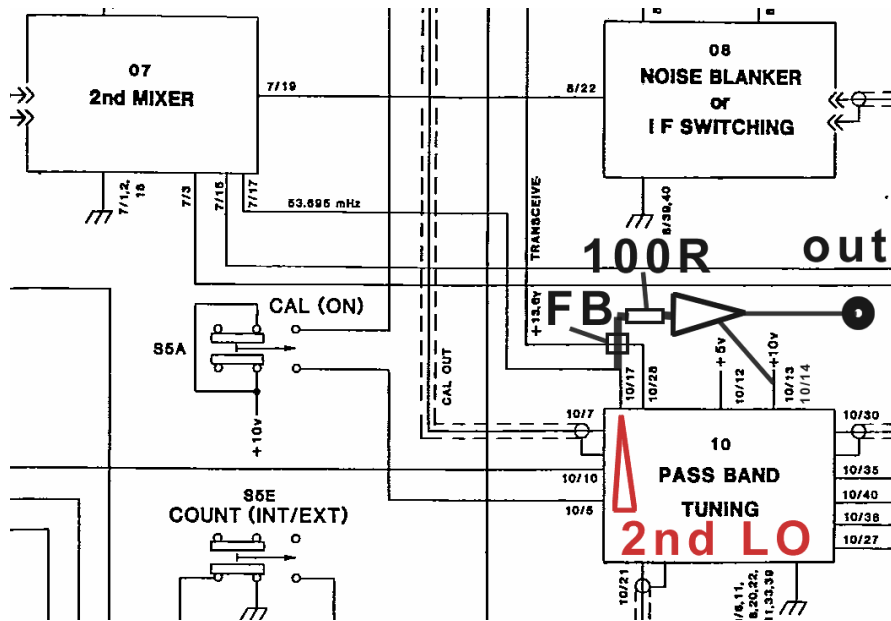


Picture 7 Connection of 2<sup>nd</sup> LO

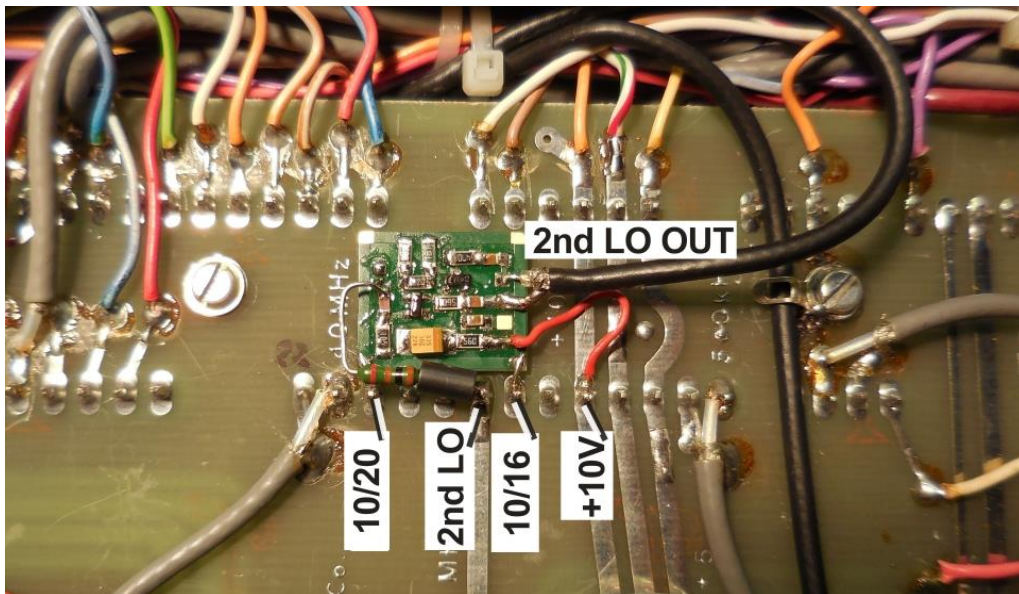To avoid any parasitic oscillations, again a ferrite bead (FB) and a 100Ohm resistor is proposed (Picture 8).



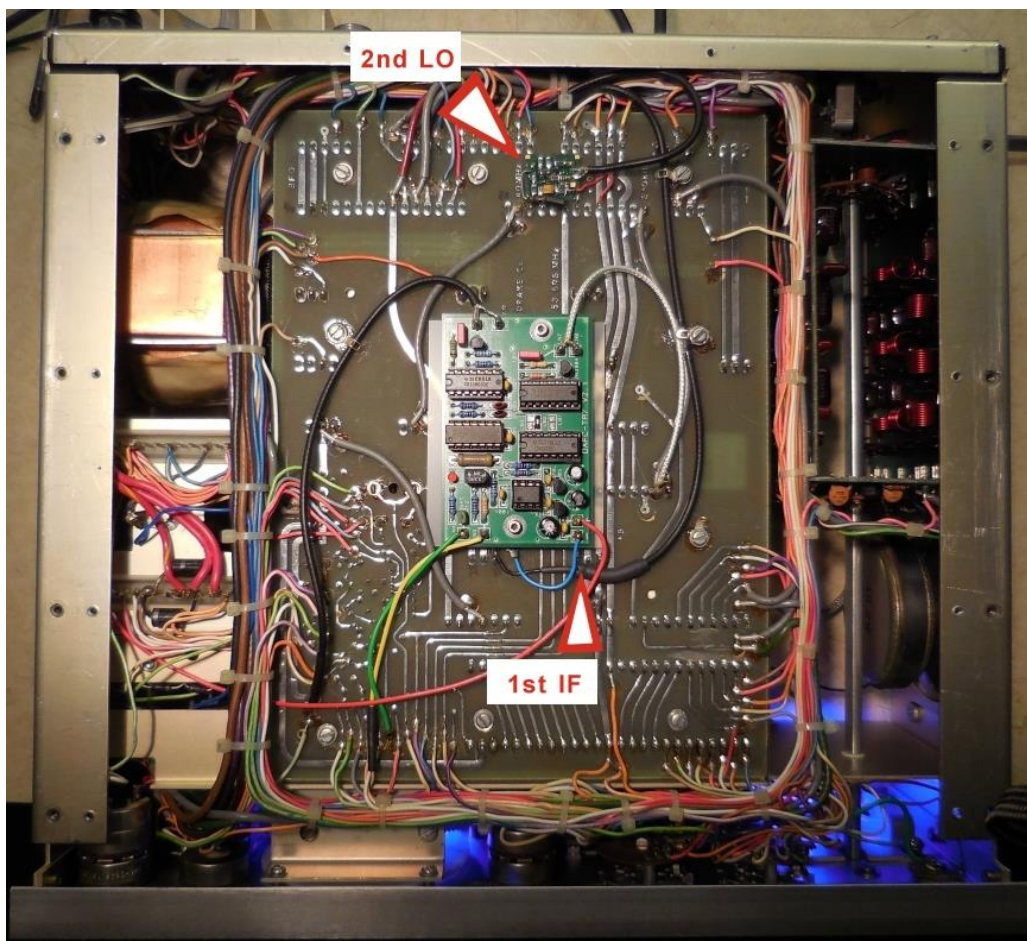Picture 8 Installation of Buffer for 2<sup>nd</sup> LO



Picture 9 Output of 1<sup>st</sup> IF and 2<sup>nd</sup> LO (family picture)

## Outputs at the R7


Two connectors are installed at the rear side of the R7 and labelled (picture 10).



Picture 10 Rear Side of R7

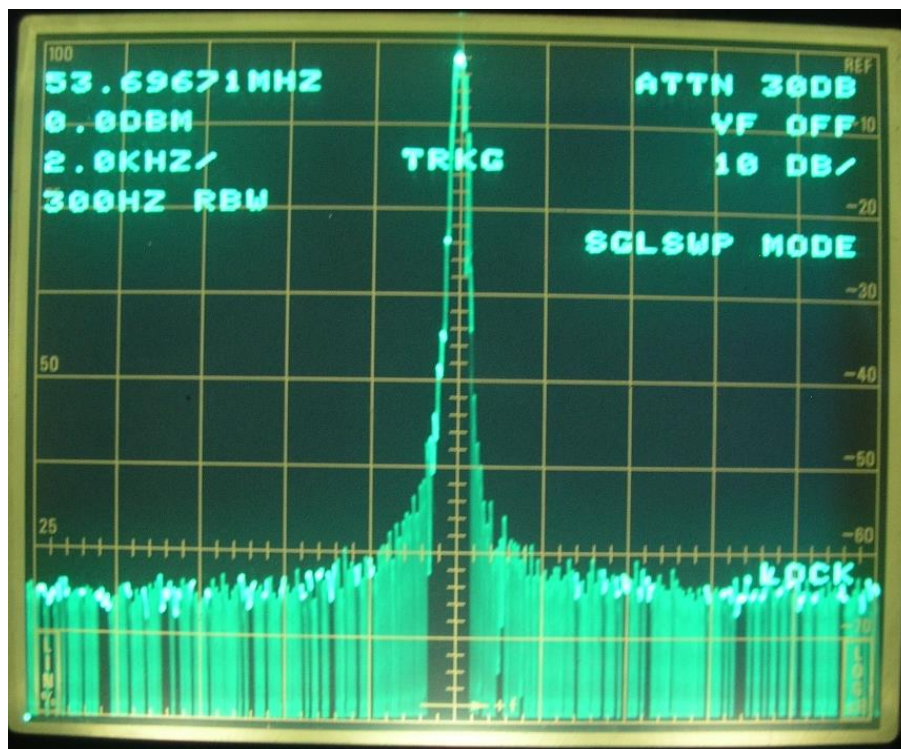
## Results (Measurements)

The 2<sup>nd</sup> LO's output is measured with app. 0dBm (picture 11) and can be used as input for an amplifier driving the external down converter.



Picture 11 Output of 2<sup>nd</sup> LO

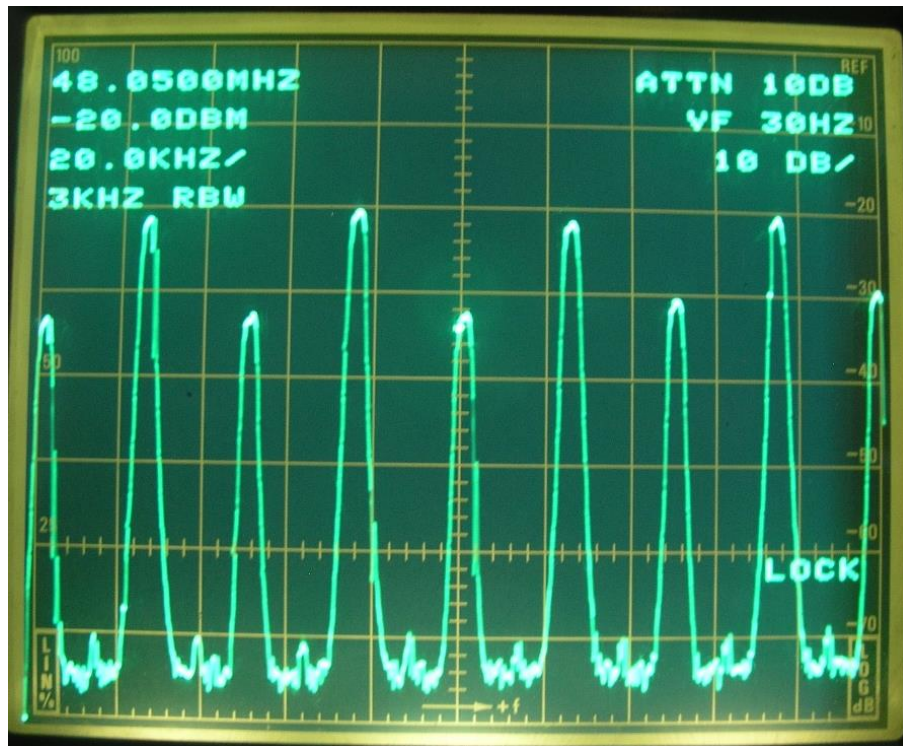The 1<sup>st</sup> IF's output at 48,05MHz (calibrator in the R7 activated) is shown in picture 12. It is important to see that the AGC of the R7 does not affect this IF-output because the AGC is active only for stages "behind". This is good for a constant output which can be calibrated in S-units. The S-meter showed S9plus for an output of -40dBm.



Picture 12 First Test with Calibrator

The last setup, connected to a small antenna, tuned to 7.100MHz (center frequency) and set to a span of +/-100kHz (20kHz/div) is shown in picture 13.



Picture 13 Complete Setup for 7MHz

Looks very nice but a little bit too expensive for permanent operation.....smile.

---

If you want to contact the author:  
 Stefan Steger, DL7MAJ, eMail: [dl7maj@darc.de](mailto:dl7maj@darc.de)  
 Homepage: [www.dl7maj.de](http://www.dl7maj.de)